

COMPUTER SYSTEMS AND ORGANIZATION

Part 1


Daniel Graham



ENGINEERING

REVIEW

THE IDEA

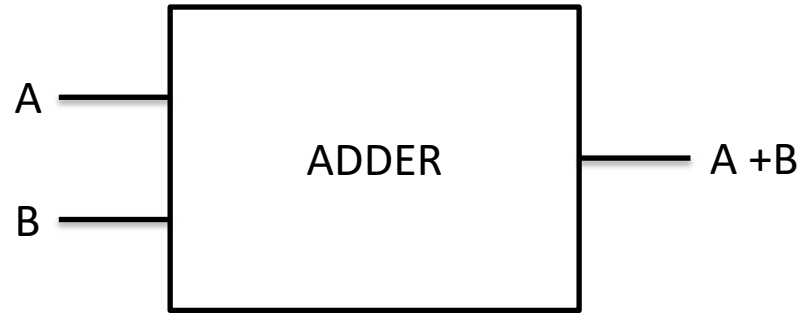

THE CHALLENGE

Our gates only support 0 and 1s.

How can we represent other decimal numbers?

How can we present negative numbers?

What about fractions 😊?

DECIMAL

- Decimal numbers

1's column
10's column
100's column
1000's column

$$5374_{10} = 5 \times 10^3 + 3 \times 10^2 + 7 \times 10^1 + 4 \times 10^0$$

five thousands three hundreds seven tens four ones

BINARY

1's column
2's column
4's column
8's column


$$1101_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 13_{10}$$

one eight one four no two one one

BINARY CONVERSION EXAMPLES


Convert 74 to binary = 1001010

$74 \div 2 = 37$	remainder 0
$37 \div 2 = 18$	remainder 1
$18 \div 2 = 9$	remainder 0
$9 \div 2 = 4$	remainder 1
$4 \div 2 = 2$	remainder 0
$2 \div 2 = 1$	remainder 0
$1 \div 2 = 1$	remainder 1




Convert 10101 to Decimal

Highest order bit Lowest order bit



1001010


4-BIT ADDER

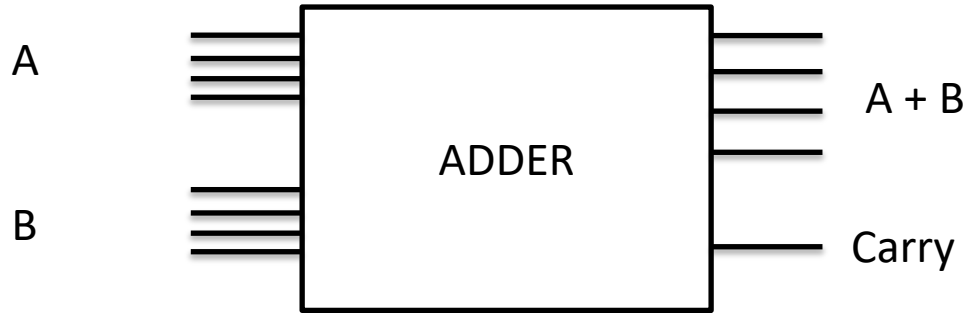

INPUTS AND OUTPUT OF OUR ADDER

What would the input be if wanted to add 5 and 9?
Notice we need to pick and order for the wires. More
on this later 😊

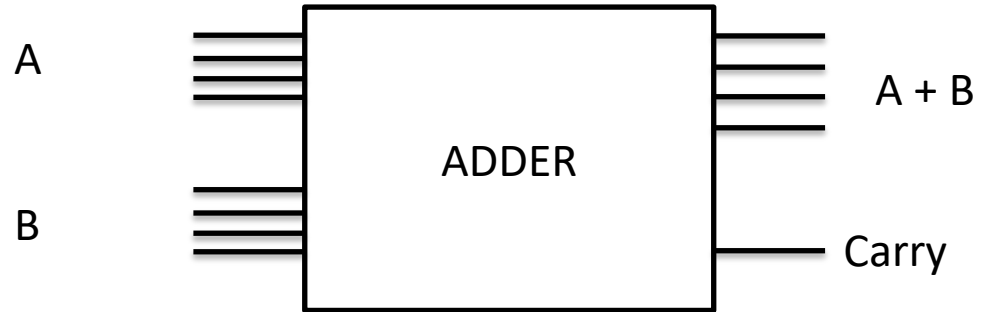
Which output lights would we want to light
Up?



INPUTS AND OUTPUT OF OUR ADDER

What if we now added 7 and 9?

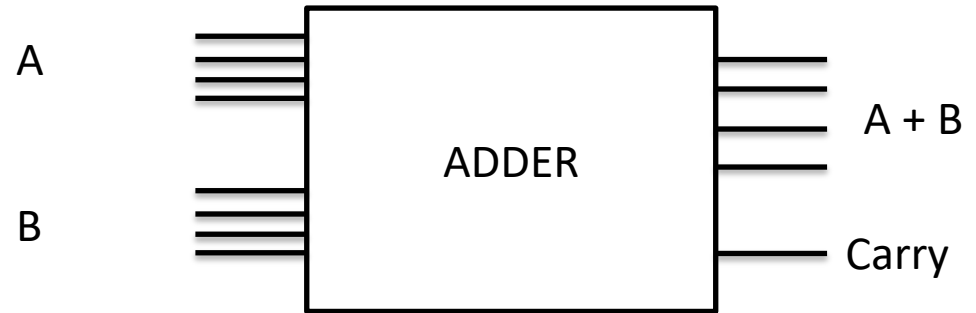What would our inputs be, and which lights do we expect to light up?



ADDING

$$\begin{array}{r} 1\ 1\ 1\ 1 \quad \leftarrow \text{Carries} \\ 0\ 1\ 1\ 1 \\ + 1\ 0\ 1\ 1 \\ \hline 0\ 0\ 1\ 0 \end{array}$$

Let's start by building a half adder something that just adds two bits.

Let's build a truth table.

A	B	A + B	C.out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

We can implement
A + B with an **XOR gate**
And the C.out (Carry out)
With an **AND gate**

ADDING


$$\begin{array}{r} 1\ 1\ 1\ 1 \quad \leftarrow \text{Carries} \\ 0\ 1\ 1\ 1 \\ + 1\ 0\ 1\ 1 \\ \hline 0\ 0\ 1\ 0 \end{array}$$

Let's start by building a half adder something that just adds two bits.


Let's build a truth table.

A	B	A + B	C.out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

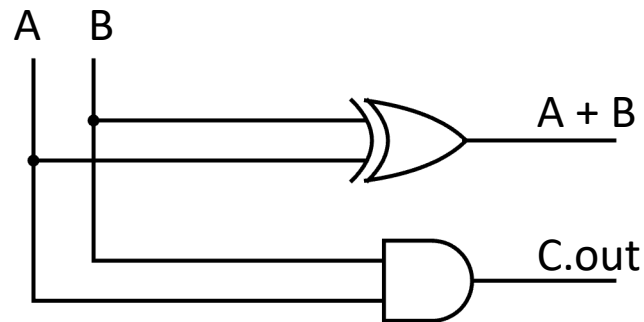We can implement
A + B with an **XOR gate**
And the C.out (Carry out)
With an **AND gate**



HALF ADDER DEMO

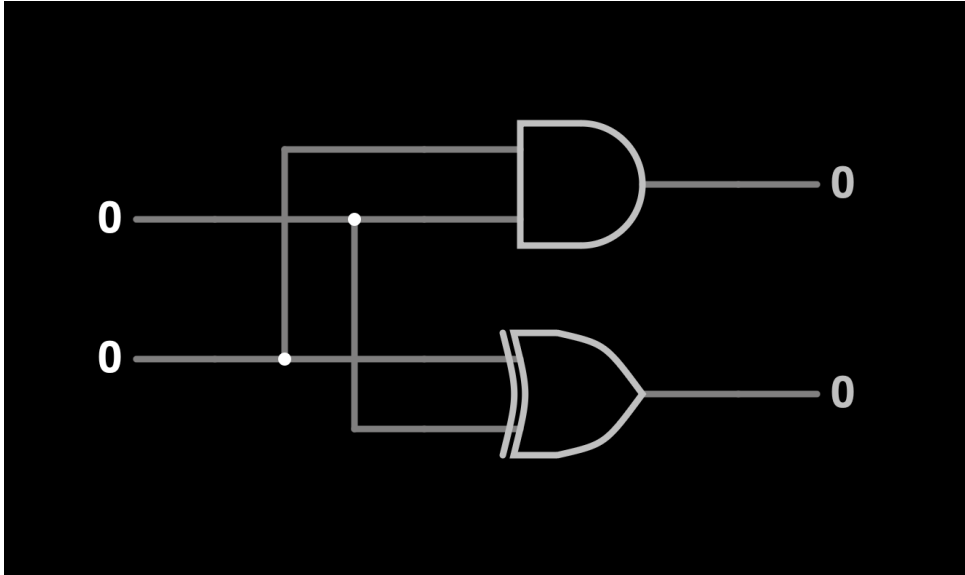


<https://tinyurl.com/ygpea8v4>

<http://www.falstad.com/circuit/circuitjs.html?ctz=CQAgjCAMB0I3BWc0FwCwCY0HYEA4cEMEIURTJyBTAWjDACgwE0QMs21KBmANj06VKGKOSZI2rMGI Z8B01sNEIGAGXAZ5vSnkphtbUQDMAhgBsAzlXJQ1GgZJC62HEZVOXRSSAwDu9lykDRx9-fWEOcIDQ8AMwTUDov1il1kcQ5PitPQBOESiYsDyU8GLiXlswsoQK9JrK0vzgyIMfAFkQOXAZEDR9brS2FAYOrqxKPtquQwxhoA>


ADDING

1 1 1 1 ← Carries
0 1 1 1
+ 1 0 1 1
0 0 1 0

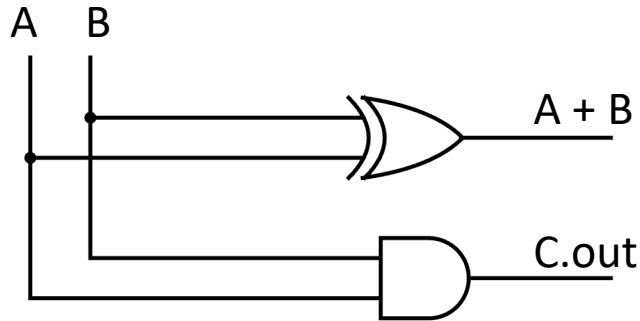We can implement
 $A + B$ with an **XOR gate**
And the C.out (Carry out)
With an **AND gate**




Half Adder

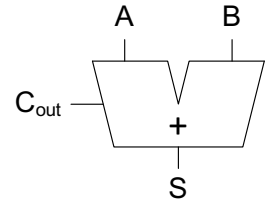

A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$
$$C_{out} = AB$$

Half Adder

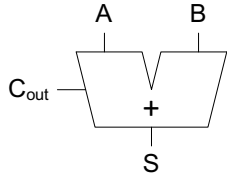


A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

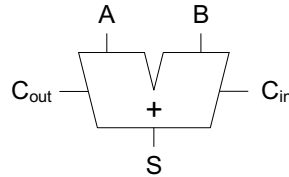


C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Note on special case 3 input xor.
 Draw the three gates. Really
 Two xors stacked.



Full Adder

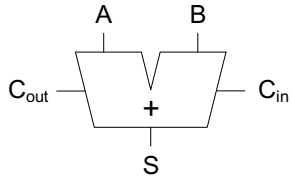

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

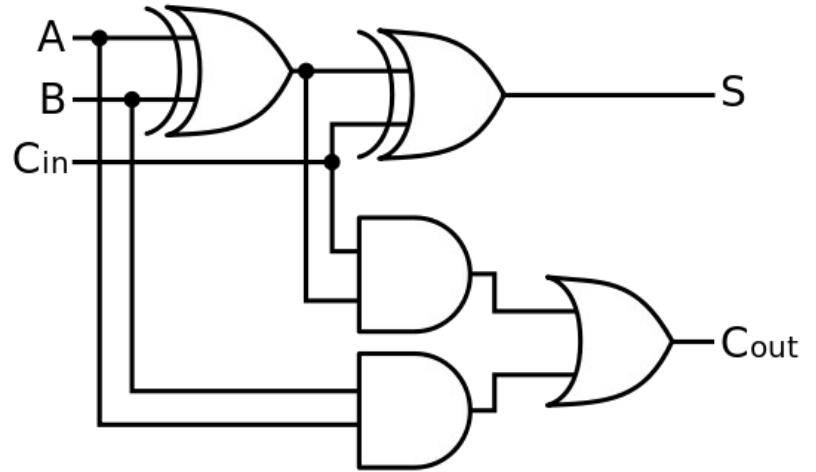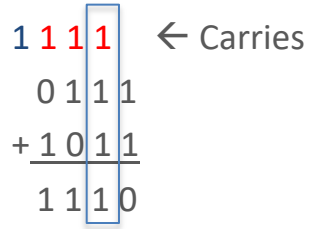


C.out has been rewritten to reduce the number of gates needed.

DEMO FULL ADDER


<https://tinyurl.com/2cfbbshs>

<http://www.falstad.com/circuit/circuitjs.html?ctz=CQAgjCAMB0I3BWc0FwCwCY0HYEA4cEMEIURTJyBTAWjDACgwE1w1WNsMRPveoeAhExYgAzGIBsPBNLSSOsgd1IMA7jy6buYyBy2R14vdvFTThjROlhJlfrqWz0rPa1uoR-p59YvGn6sYOw8-s4OdqYY4d54eOAYCfLBSV4AsuQAnNyOIJL+eXwoRvR88WwcFc4hwWDceJRIASCN4PWt9krObcQ2oX1eADKdMnIJg7kgAGYAhgA2AM5U5MPt5ckTFVNzSytIhiO1YaxoE-47C8urNaHHzcc1HfcdSQnOKYnJCpUt1uA5YzBQH OXTAnQmfgfH6DBDYVzdlxwhHSZE8SDvBiZNEYDH5C544rCZhNO5pN5fZSrYlKf5geEgT706T2IQibhMqlIQF5VmqlA>

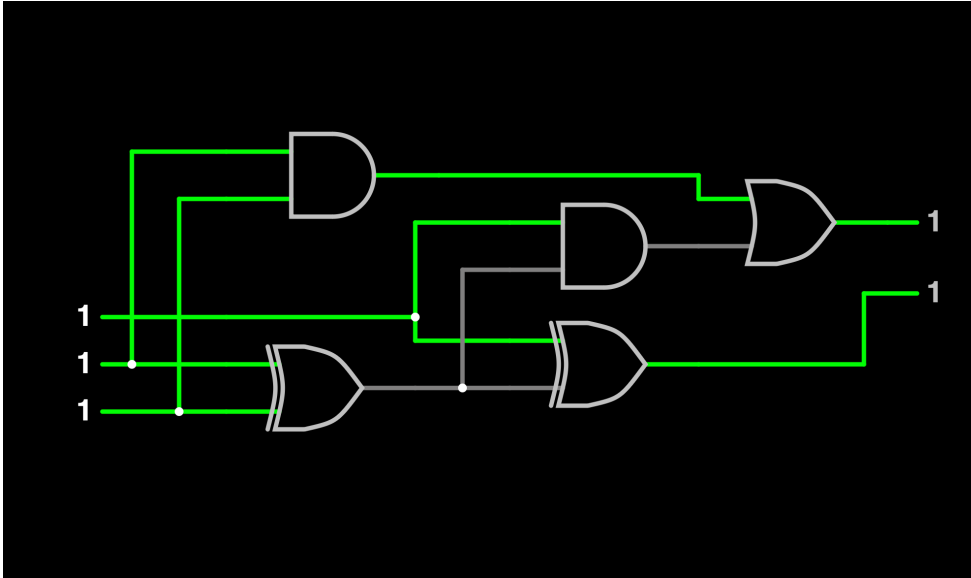

RIPPLE CARRY ADDER

Next let's build a full adder

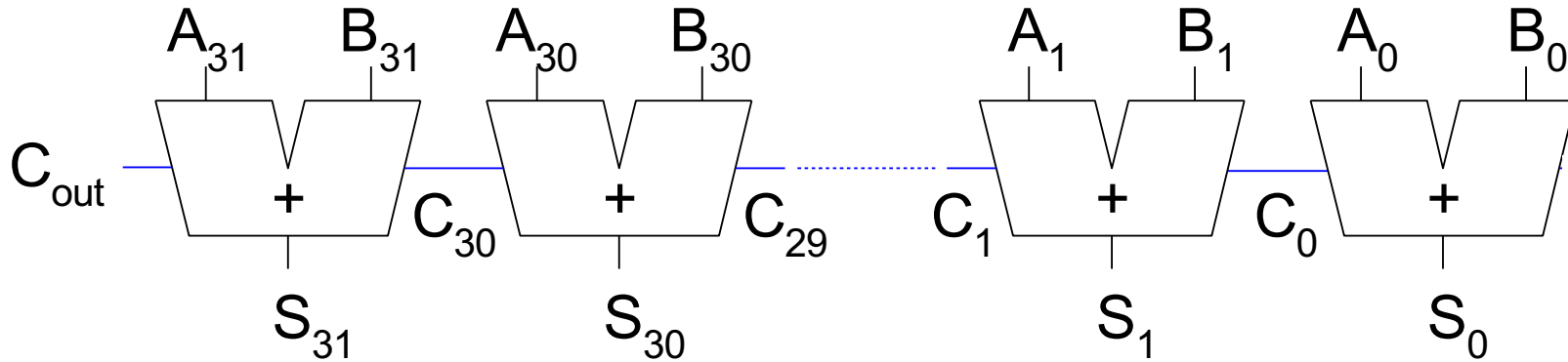



RIPPLE CARRY ADDER

1 1 1 1 ← Carries

0 1 1 1
+ 1 0 1 1

0 0 1 0

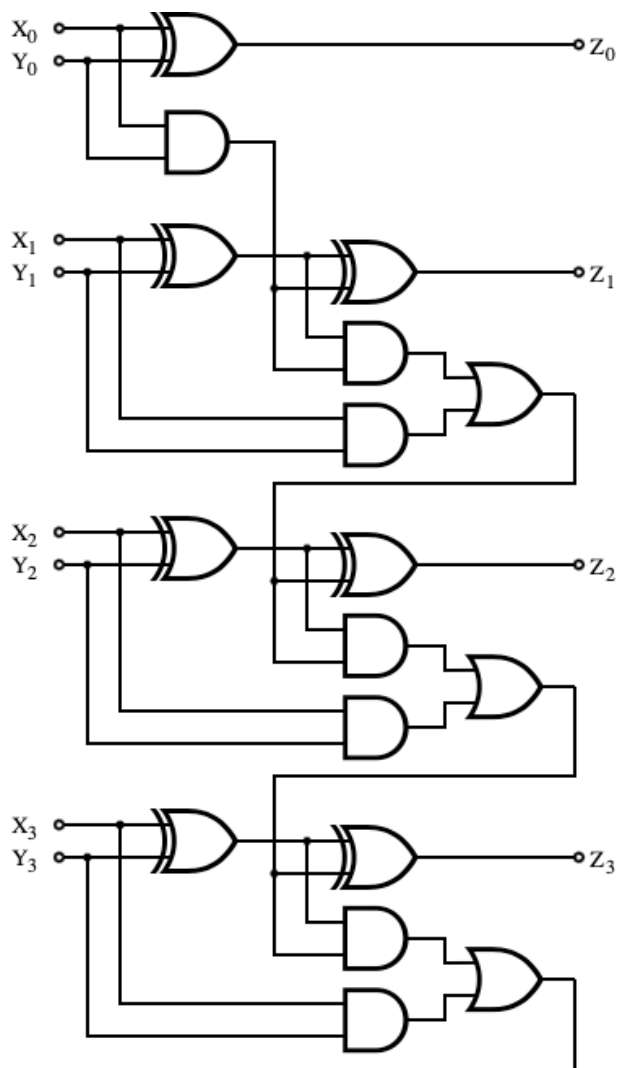


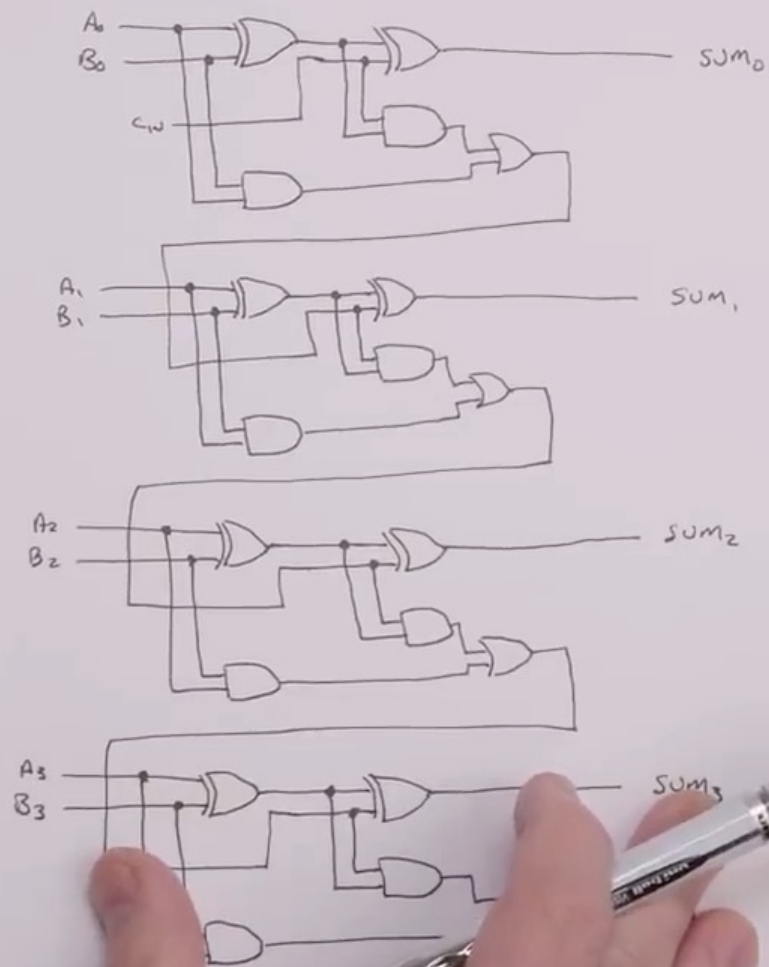

CHALLENGE CAN WE BUILD A CIRCUIT THAT INCREMENTS A NUMBER BY ONE

Page 5: Circuits

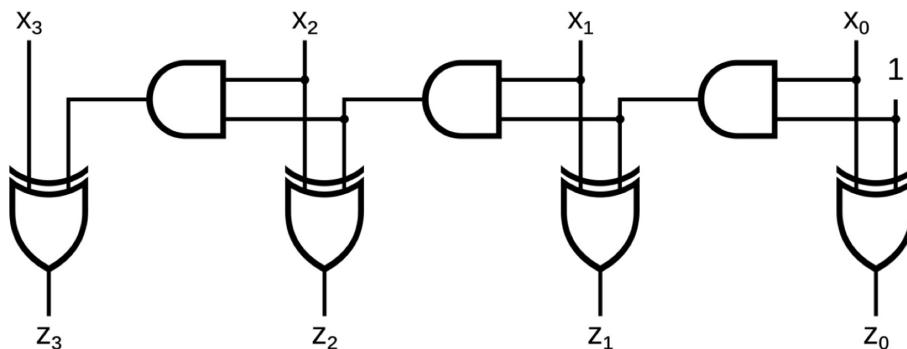10. [16 points] In class, we discussed a 4-bit increment circuit below that added 1 to the input.



How can we change this circuit to instead increment by 2, i.e., $x += 2$? Draw the new circuit below. *Note: you should not use more gates than the original circuit.*

